

Complete the key for the electrical symbols.



Draw a circuit diagram for a battery linked to a switch and bulb. Remember the symbols must be linked by straight lines and the diagram drawn in the shape of a box.