

Task Sheet 2

Name _____

Date _____

Match each sentence to the correct circuit diagram.

- 1 Bell working without a switch = diagram _____
- 2 Bulb working without a switch = diagram _____
- 3 Motor working with a switch = diagram _____
- 4 Buzzer working with a switch = diagram _____
- 5 Bell working with a switch = diagram _____
- 6 Two bulbs working with a switch = diagram _____

