

Circuit Diagrams.

Draw a circuit diagram beside each sentence to match each description.

1 Bell working without a switch

2 Bell working with a switch

3 Motor working with a switch

4 Buzzer working with a switch

5 Lamp working without a switch

6 Two lamps working with a switch