











Name .....

Date .....
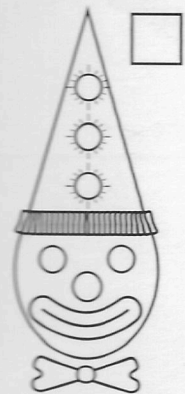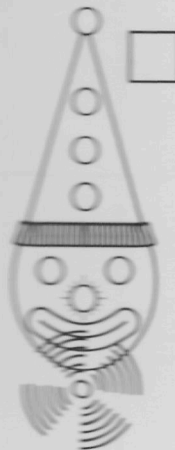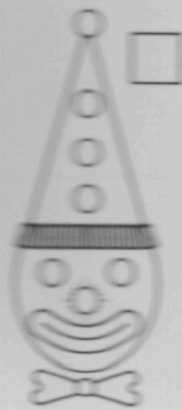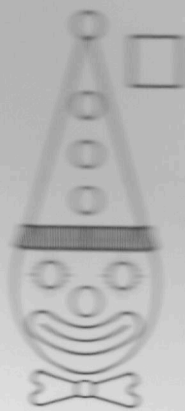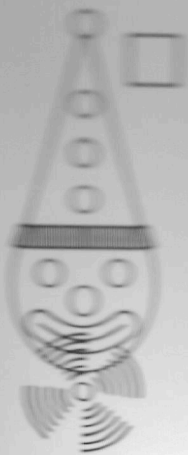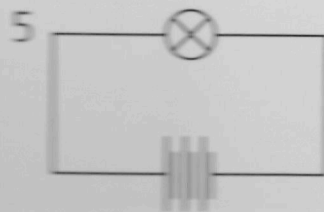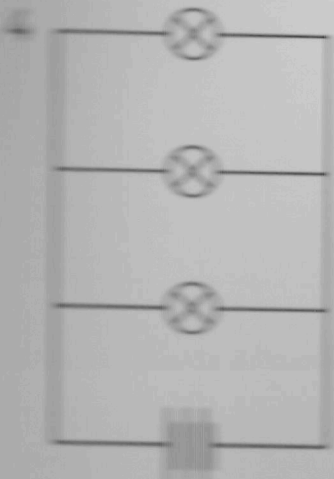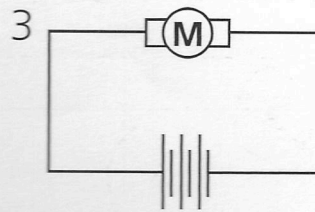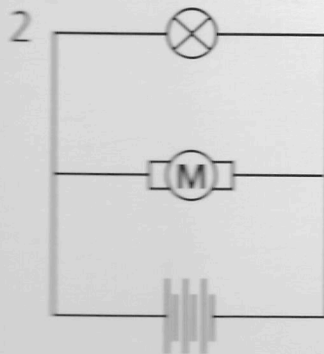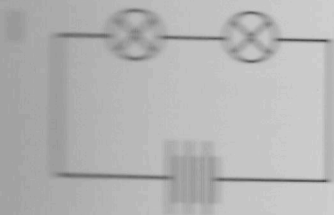
## Matching circuit diagrams

Match the correct circuit diagram to the clown.

Put the circuit diagram number in the box next to each clown.



Bow tie spins round

Eyes light up

Nose lights up

Nose lights up and bow tie spins round

Lights on hat light up