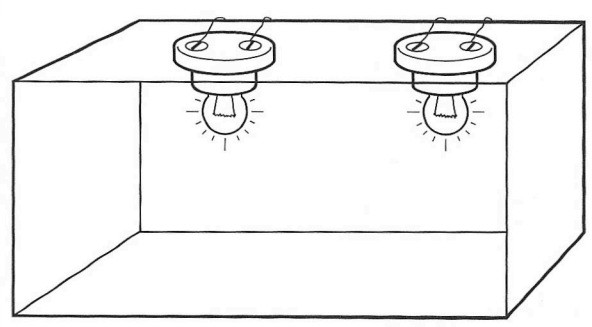


Name



Date

Which components?



Some children made models of rooms in a house.
They used different components in each room.
Draw the correct circuit diagram for each room.



• two ceiling lights

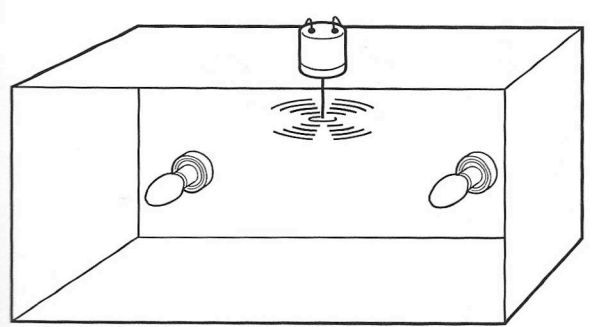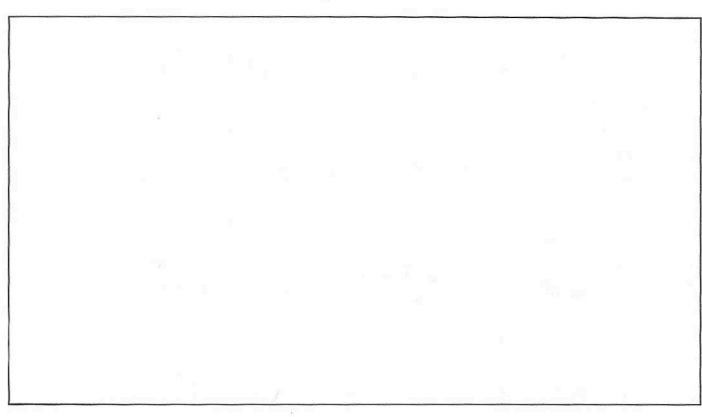

• a ceiling fan and wall lights

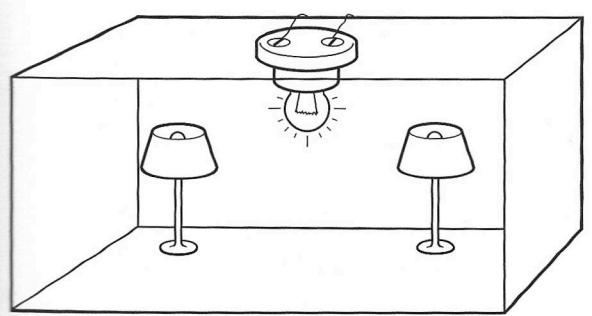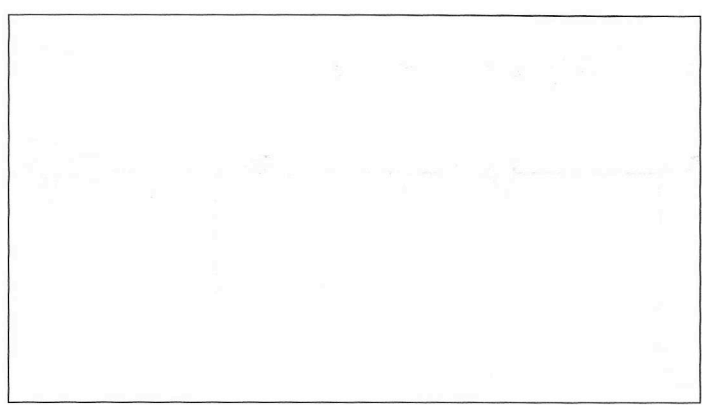

• a ceiling light and two standard lamps

