

## **DETERMINATION OF THE INTERNAL RESISTANCE OF A CELL**

**Specification reference:** AS Unit 2.3 – D.C. circuits

### **Theory:**


The equation used for determining the internal resistance is  $V = E - Ir$  where  $V$  is the terminal p.d. of a cell;  $E$  is the emf of the cell;  $I$  the current flowing in the circuit and  $r$  is the internal resistance.  $V = IR$  and the equation can be re-written as  $R = \frac{E}{I} - r$ . Therefore a graph of  $R$  against  $\frac{1}{I}$  should be linear.

### **Apparatus:**

Cells – e.g. 3 or 4  $\times$  1.5 V “D” type batteries connected in series  
 Switch  
 Ammeter or multimeter set to A range -  $\pm 0.01$  A  
 Various resistor values 0 -  $60\ \Omega$

### **Experimental method:**

The circuit should be set-up as follows:

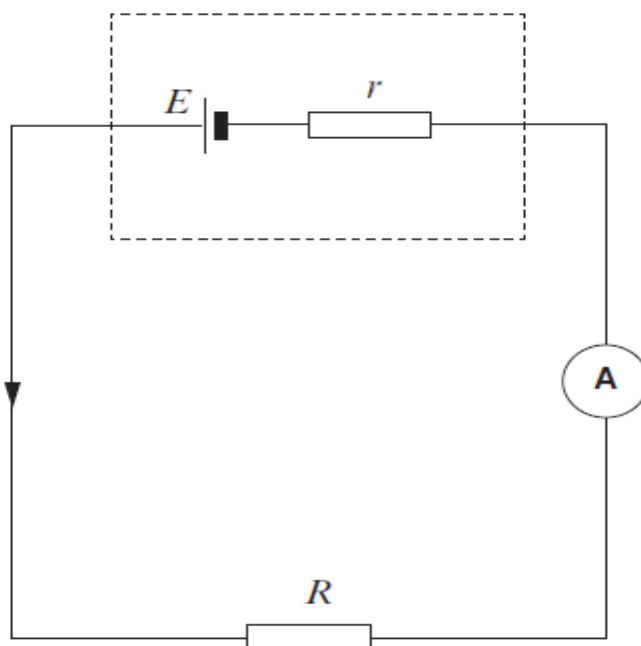

The resistor values should be varied and the current values recorded. Plot a graph of  $R$  ( $y$ -axis) against  $\frac{1}{I}$  ( $x$ -axis). The graph should be a straight line with the intercept on the  $y$ -axis which is equal to the value of the internal resistance.

**Extension:**

The current can also be varied and the terminal potential difference measured. A graph of potential difference against current should be linear and the emf of the cell could be determined.

**Practical Techniques:**

- Use appropriate analogue apparatus to record a range of measurements (to include length/distance, temperature, pressure, force, angles, volume) and to interpolate between scale markings.
- Use calipers and micrometers for small distances, using digital or vernier scales.
- Correctly construct circuits from circuit diagrams using D.C. power supplies, cells, and a range of circuit components, including those where polarity is important.
- Use ICT such as computer modelling, or data logger with a variety of sensors to collect data, or use of software to process data.

**Relevant previous practical past papers:**

- PH3 2007 Q2
- PH3 2011 Task B4